

Digital Logic Circuits 'Boolean Algebra' ELEC2200 Summer 2009

David J. Broderick

brodedj@auburn.edu

<http://www.auburn.edu/~brodedj>

Office: Broun 360



Boolean Algebra


- Developed by George Boole of Bell Labs (1849)
- Originally termed Switching Algebra as it described the math of relay circuits
- Classical Algebra manipulates expressions comprised of real-valued variables and joined by operators such as: Add, Subtract, Multiply, Divide
- Boolean Algebra manipulates expressions comprised of binary-valued variables and joined by operators such as: And, Or, Not
- Other operators can be built from these




Boolean Attributes (Operators)

- Complement, Invert, Not
- Two notations: A' and \bar{A}
- And
- Notated as $A \cdot B$

A	\bar{A}
0	1
1	0

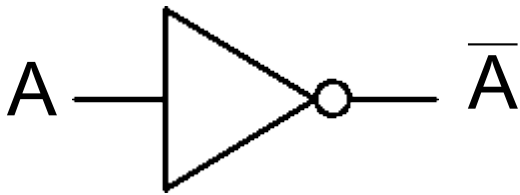


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

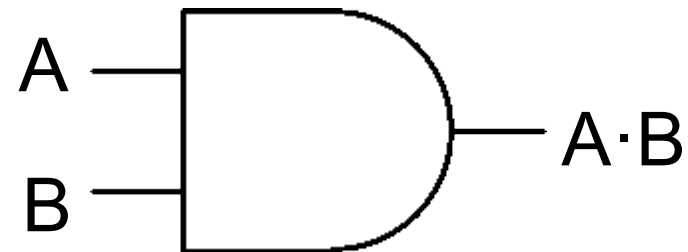

Boolean Attributes (Operators)

- Or
- Notated as $A+B$

A	B	$A+B$
0	0	0
0	1	1
1	0	1
1	1	1

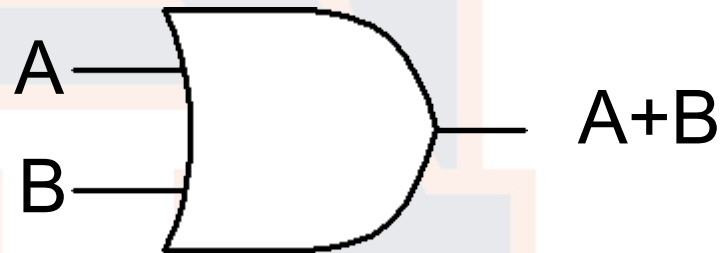

Operator Precedence

- Order:
 - (1) Parentheses
 - (2) Not
 - (3) And
 - (4) Or
 - (5) Left to Right
- When in doubt, use parentheses.



Boolean Postulates

- Identity

$$A+0=A$$

$$A \cdot 1=A$$

A	B	$A+0$
0	0	0
0	1	1
1	0	1
1	1	1

- Complements

$$A+\bar{A}=1$$

$$A \cdot \bar{A}=0$$

A	B	$A \cdot 1$
0	0	0
0	1	0
1	0	0
1	1	1

A	B	$A+\bar{A}$
0	0	0
0	1	1
1	0	1
1	1	1

A	B	$A \cdot \bar{A}$
0	0	0
0	1	0
1	0	0
1	1	1



Boolean Postulates

- Commutativity

$$A+B=B+A$$

$$A \cdot B = B \cdot A$$

A	B	A+B	B+A
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	1

A	B	A·B	B·A
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A+B
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A+B	(A+B)+C
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A+B	(A+B)+C	B+C
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A+B	(A+B)+C	B+C	A+(B+C)
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	0	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A+B	(A+B)+C	B+C	A+(B+C)
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	1	0	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	A · B
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	$A \cdot B$	$(A \cdot B) \cdot C$
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	1	0
1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	$A \cdot B$	$(A \cdot B) \cdot C$	$B \cdot C$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	0
1	1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	$A \cdot B$	$(A \cdot B) \cdot C$	$B \cdot C$	$A \cdot (B \cdot C)$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	0
1	1	1	1	1	1	1



Boolean Postulates

- Associativity

$$(A+B)+C=A+(B+C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

A	B	C	$A \cdot B$	$(A \cdot B) \cdot C$	$B \cdot C$	$A \cdot (B \cdot C)$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	0	0	0	0
1	1	0	1	0	0	0
1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B	A+C
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B	A+C	(A+B)·(A+C)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	1	1	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B	A+C	(A+B)·(A+C)	B·C
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	1	0	0	0
0	1	1	1	1	1	1
1	0	0	1	1	1	0
1	0	1	1	1	1	0
1	1	0	1	1	1	0
1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B	A+C	(A+B)·(A+C)	B·C	A+(B·C)
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A+B	A+C	$(A+B) \cdot (A+C)$	B · C	A+(B · C)
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A·B
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	A·B	A·C
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	$A \cdot B$	$A \cdot C$	$(A \cdot B) + (A \cdot C)$
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	$A \cdot B$	$A \cdot C$	$(A \cdot B) + (A \cdot C)$	$B+C$
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	1
0	1	1	0	0	0	1
1	0	0	0	0	0	0
1	0	1	0	1	1	1
1	1	0	1	0	1	1
1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	$A \cdot B$	$A \cdot C$	$(A \cdot B)+(A \cdot C)$	$B+C$	$A \cdot (B+C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	0
0	1	1	0	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1
1	1	0	1	0	1	1	1
1	1	1	1	1	1	1	1



Boolean Postulates

- Distributivity

$$A+(B \cdot C)=(A+B) \cdot (A+C)$$

$$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$$

A	B	C	$A \cdot B$	$A \cdot C$	$(A \cdot B)+(A \cdot C)$	$B+C$	$A \cdot (B+C)$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	0	1	0
0	1	1	0	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1
1	1	0	1	0	1	1	1
1	1	1	1	1	1	1	1



Boolean Theorems

- Idempotency

$$A+A=A$$

$$A \cdot A=A$$

- Null Elements

$$A+1=1$$

$$A \cdot 0=0$$

- Involution

$$\overline{\overline{A}}=(A')'=A$$

A	A+A	A·A	A+1	A·0	\overline{A}	$\overline{\overline{A}}$
0	0	0	1	0	1	0
1	1	1	1	0	0	1



Boolean Theorems

- Absorption (Covering)

$$A \cdot (A+B) = A$$

$$A + (A \cdot B) = A$$

A	B	A+B	A·B	A·(A+B)	A+(A·B)
0	0	0	0	0	0
0	1	1	0	0	0
1	0	1	0	1	1
1	1	1	1	1	1



Boolean Theorems

- Absorption (Covering)

$$A \cdot (\bar{A} + B) = A \cdot B$$

$$A + (\bar{A} \cdot B) = A + B$$

A	B	\bar{A}	$\bar{A} + B$	$A \cdot (\bar{A} + B)$	$A \cdot B$	$\bar{A} \cdot B$	$A + (\bar{A} \cdot B)$	$A + B$
0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	1	1	1
1	0	0	0	0	0	0	1	1
1	1	0	1	1	1	0	1	1



Boolean Theorems

- Absorption (Combining)

$$(A+B) \cdot (A+\bar{B}) = A$$

$$(A \cdot B) + (A \cdot \bar{B}) = A$$

A	B	\bar{B}	A+B	A+ \bar{B}	$(A+B) \cdot (A+\bar{B})$	A·B	A· \bar{B}	$(A \cdot B) + (A \cdot \bar{B})$
0	0	1	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0
1	0	1	1	1	1	0	1	1
1	1	0	1	1	1	1	0	1



Boolean Theorems

- Absorption (Combining)

$$(A \cdot B) + (A \cdot \bar{B} \cdot C) = (A \cdot B) + (A \cdot C)$$

$$(A + B) \cdot (A + \bar{B} + C) = (A + B) \cdot (A + C)$$

A	B	C	\bar{B}	$A \cdot B$	$A \cdot \bar{B} \cdot C$	$A \cdot C$	$(A \cdot B) + (A \cdot \bar{B} \cdot C)$	$(A \cdot B) + (A \cdot C)$
0	0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0
1	0	1	1	0	1	1	1	1
1	1	0	0	1	0	0	1	1
1	1	1	0	1	0	1	1	1



Boolean Theorems

- Absorption (Combining)

$$(A \cdot B) + (A \cdot \bar{B} \cdot C) = (A \cdot B) + (A \cdot C)$$

$$(A+B) \cdot (A+\bar{B}+C) = (A+B) \cdot (A+C)$$

A	B	C	\bar{B}	A+B	A+ \bar{B} +C	A+C	$(A+B) \cdot (A+\bar{B}+C)$	$(A+B) \cdot (A+C)$
0	0	0	1	0	1	0	0	0
0	0	1	1	0	1	1	0	0
0	1	0	0	1	0	0	0	0
0	1	1	0	1	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1
1	1	1	0	1	1	1	1	1



Boolean Theorems

- DeMorgan's Theorem

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- Break the bar and change the operator
- Connect the bar and change the operator
- Expands to include more terms (Generalized DeMorgan's):

$$\overline{A+B+C+\dots} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \dots$$

$$\overline{A \cdot B \cdot C \cdot \dots} = \overline{A} + \overline{B} + \overline{C} + \dots$$



Boolean Theorems

- DeMorgan's Theorem

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

A	B	A+B	A·B	$\overline{A+B}$	$\overline{A \cdot B}$	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{A} + \overline{B}$
0	0	0	0	1	1	1	1	1	1
0	1	1	0	0	1	1	0	0	1
1	0	1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0	0	0



Boolean Theorems

- Consensus Theorem
- $(A \cdot B) + (\bar{A} \cdot C) + (B \cdot C) = (A \cdot B) + (\bar{A} \cdot C)$
- $(A + B) \cdot (\bar{A} + C) \cdot (B + C) = (A + B) \cdot (\bar{A} + C)$

A	B	C	\bar{A}	$A \cdot B$	$\bar{A} \cdot C$	$B \cdot C$	$(A \cdot B) + (\bar{A} \cdot C) + (B \cdot C)$	$(A \cdot B) + (\bar{A} \cdot C)$
0	0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	1	1
0	1	0	1	0	0	0	0	0
0	1	1	1	0	1	1	1	1
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	1	0	0	1	1
1	1	1	0	1	1	1	1	1



Boolean Theorems

- Consensus Theorem
- $(A \cdot B) + (\bar{A} \cdot C) + (B \cdot C) = (A \cdot B) + (\bar{A} \cdot C)$
- $(A+B) \cdot (\bar{A}+C) \cdot (B+C) = (A+B) \cdot (\bar{A}+C)$

A	B	C	\bar{A}	A+B	$\bar{A}+C$	B+C	$(A+B) \cdot (\bar{A}+C) \cdot (B+C)$	$(A+B) \cdot (\bar{A}+C)$
0	0	0	1	0	1	0	0	0
0	0	1	1	0	1	1	0	0
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	1	1	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	1	1	1
1	1	0	0	1	0	1	0	0
1	1	1	0	1	1	1	1	1



Boolean Theorems

- Shannon's Expansion

$$f(A,B,C)=(A \cdot f(1,B,C))+(\bar{A} \cdot f(0,B,C))$$

$$f(A,B,C)=(A+f(0,B,C)) \cdot (\bar{A}+f(1,B,C))$$

- Example:

$$f(A,B,C)=A \cdot B \cdot C+A \cdot \bar{B} \cdot C+\bar{A} \cdot \bar{B} \cdot C$$

$$f(A,B,C)=A \cdot f(1,B,C)+\bar{A} \cdot f(0,B,C)$$

$$f(1,B,C)=B \cdot C+\bar{B} \cdot C$$

$$f(0,B,C)=\bar{B} \cdot C$$

$$f(A,B,C)=A \cdot (B \cdot C+\bar{B} \cdot C)+\bar{A} \cdot (\bar{B} \cdot C)$$

- Important for circuit minimization



Duality Principle

- Any theorem or postulate in Boolean Algebra remains true if
 - 0 and 1 are swapped and
 - AND and OR are swapped
- Postulates:

Postulate	Dual Pairs	
Identity	$A+0=A$	$A \cdot 1=A$
Complements	$A+\bar{A}=1$	$A \cdot \bar{A}=0$
Commutativity	$A+B=B+A$	$A \cdot B=B \cdot A$
Associativity	$(A+B)+C=A+(B+C)$	$(A \cdot B) \cdot C=A \cdot (B \cdot C)$
Distributivity	$A+(B \cdot C)=(A+B) \cdot (A+C)$	$A \cdot (B+C)=(A \cdot B)+(A \cdot C)$

Duality Principle


- Theorems

Theorem	Dual Pairs	
Idempotency	$A+A=A$	$A \cdot A=A$
Null Elements	$A+1=1$	$A \cdot 0=0$
Involution	$\overline{\overline{A}}=A$	$\overline{\overline{A}}=A$
Covering	$A+(A \cdot B)=A$	$A \cdot (A+B)=A$
Covering	$A+(\overline{A} \cdot B)=A+B$	$A \cdot (\overline{A}+B)=A \cdot B$
Combining	$(A \cdot B)+(A \cdot \overline{B})=A$	$(A+B) \cdot (A+\overline{B})=A$
Combining	$(A \cdot B)+(A \cdot \overline{B} \cdot C)=(A \cdot B)+(A \cdot C)$	$(A+B) \cdot (A+\overline{B}+C)=(A+B) \cdot (A+C)$
DeMorgan's	$\overline{A+B}=\overline{A} \cdot \overline{B}$	$\overline{A \cdot B}=\overline{A}+\overline{B}$
Consensus	$(A \cdot B)+(\overline{A} \cdot C)+(B \cdot C)=(A \cdot B)+(\overline{A} \cdot C)$	$(A+B) \cdot (\overline{A}+C) \cdot (B+C)=(A+B) \cdot (\overline{A}+C)$
Shannon's	$f(A,B,C)=A \cdot f(1,B,C)+\overline{A} \cdot f(0,B,C)$	$f(A,B,C)=A+f(0,B,C) \cdot \overline{A}+f(1,B,C)$




Switching Functions

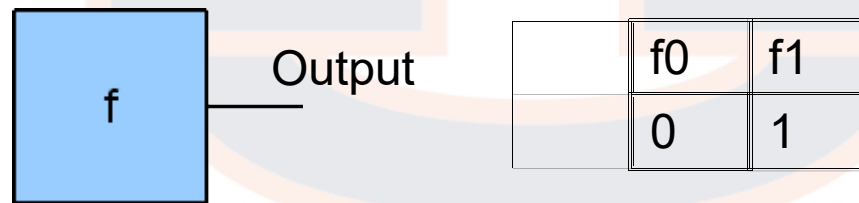- We've shown proof that two expressions are equivalent by testing every possible input
- We can also generate every expression given the # of inputs, n
- The simplest (trivial) case, $n=0$, or no inputs:



Switching Functions


- 1 input, $n=1$

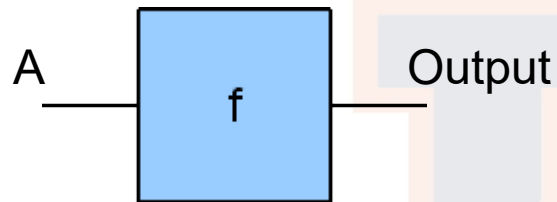


A	f0	f1	f2	f3
0	0	1	0	1
1	0	0	1	1

Function	Expression	Description
f0	0	Logic 0
f1	\bar{A}	Inverter
f2	A	Buffer
f3	1	Logic 1

Inverter

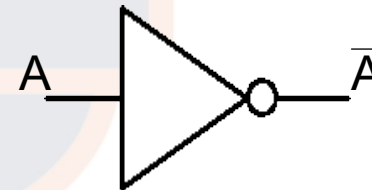


Buffer

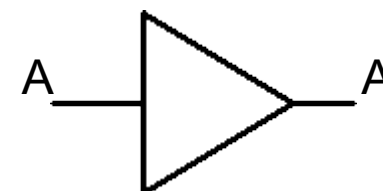

Switching Functions

- 2 inputs, $n=2$

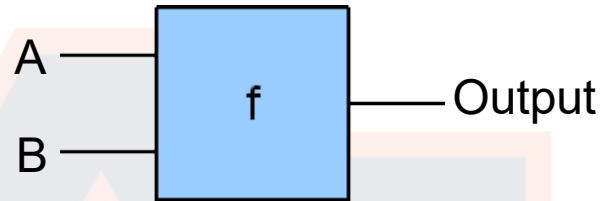


A	B	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f
		0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- Looking closely, we've seen some of these before



Switching Functions

- 2 inputs, $n=2$

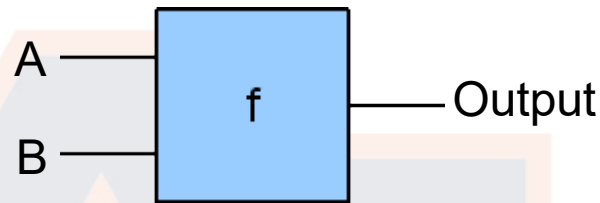


A	B	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- These are the two trivial logic sources
 - $f_0 = 0$
 - $f_F = 1$



Switching Functions

- 2 inputs, $n=2$

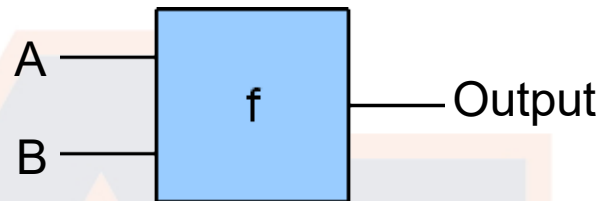


A	B	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f	f
0	0	0	1	0	1	0	1	0	1	0	1	A	B	C	D	E	F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- f_C and f_A are buffers for A and B respectively
- f_3 and f_5 are inverters for A and B respectively



Switching Functions

- 2 inputs, $n=2$

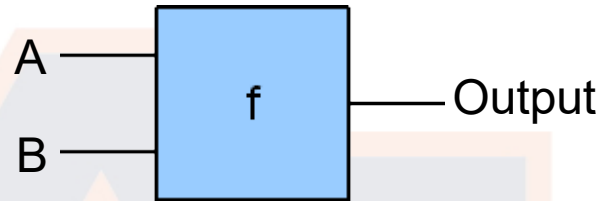


A	B	f ₀	f ₁	f ₂	f ₃	f ₄	f ₅	f ₆	f ₇	f ₈	f ₉	A	B	C	D	f _E	f _F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- f_E is $A+B$
- f_8 is $A \cdot B$



Switching Functions

- 2 inputs, $n=2$

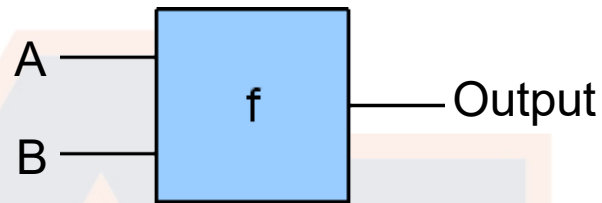


A	B	f	f	f	f	f	f	f	f	f	f	A	B	C	D	E	F
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- f_1 is $\overline{A+B}$, NOR
- f_7 is $\overline{A \cdot B}$, NAND




New Operators

- NOR

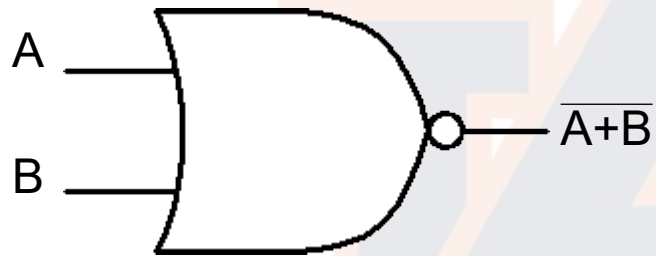

A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

- NAND

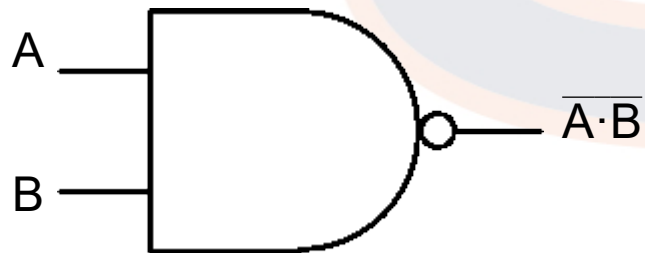


A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0



Switching Functions

- 2 inputs, $n=2$

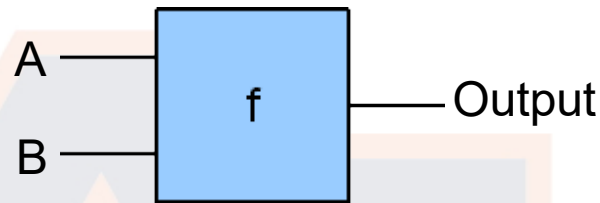


A	B	f	f	f	f	f	f	f	f	f	f	A	B	C	D	E	F
		0	1	2	3	4	5	6	7	8	9						
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

- f_6 , Exclusive OR, XOR
- f_9 , Exclusive NOR, XNOR




New Operators

- XOR

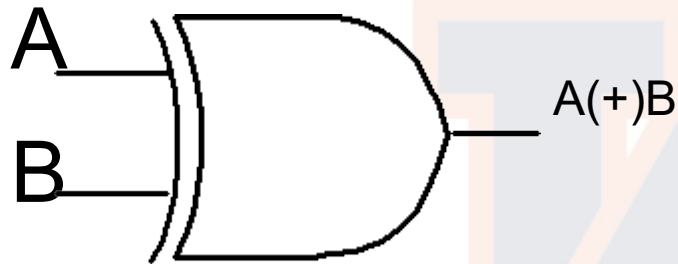

A	B	$A(+)B$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

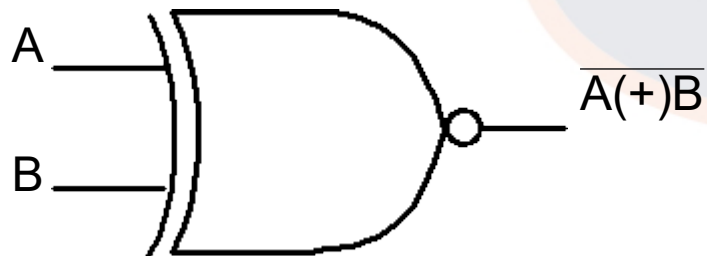

A	B	$\overline{A(+)B}$
0	0	1
0	1	0
1	0	0
1	1	1



Switching Function, n=2

Function	Expression	Description
f0	0	Logic 0
f1	$\overline{A+B}$	NOR
f2	$\overline{A \cdot B}$	
f3	\overline{A}	Inverter A
f4	$A \cdot \overline{B}$	
f5	\overline{B}	Inverter B
f6	$A(+)B$	XOR
f7	$\overline{A \cdot B}$	NAND
f8	$A \cdot B$	AND
f9	$\overline{A(+)B}$	XNOR
fA	B	Buffer B
fB	$\overline{A+B}$	
fC	A	Buffer A
fD	$A+\overline{B}$	
fE	$A+B$	OR
fF	1	Logic 1



Switching Functions

- How many possible functions given # of inputs, n ?
 - $n=0$, 2 functions
 - $n=1$, 4 functions
 - $n=2$, 16 functions
- In general there are 2^{2^n} functions
- So for $n=3$ there are 256 possible functions

